

3/29/10

Effective Resistance

$$R(a \leftrightarrow z) = \frac{W(a) - W(z)}{\|I\|}$$

Independent of W . — get same value for any choice of voltage.

P9.5

For any $a, z \in \Omega$

$$P_a(\tau_z < \tau_a^+) = \frac{1}{c(a)R(a \leftrightarrow z)}$$

Probability that z is
visited before a return
to a — escape probability.

Proof

Function

$$x \mapsto E_x \mathbb{1}_{\{X_{\tau(a,z)} = z\}} = P_x(\tau_z < \tau_a)$$

time to visit
 a or z

Proof

Function

$$x \mapsto E_x 1_{\{X_{\tau(a,z)} = z\}} = P_x(\tau_z < \tau_a)$$

time to visit
a or z

is the unique function that is harmonic on $\Omega \setminus \{a, z\}$ and takes value 0 at a & 1 at z .

But

$$x \mapsto \frac{W(a) - W(x)}{W(a) - W(z)}$$

satisfies

uses harmonicity
of W .

S o,

$$P_n \{ \tau_z < \tau_a \} = \frac{W(a) - W(z)}{W(a) - W(z)}.$$

S o

$$P_a(\tau_z < \tau_a^+) = \sum_{n \in V} P(a, n) P_n(\tau_z < \tau_a)$$

$$= \sum_{x \sim a} \frac{c(a, x)}{c(a)} \cdot \frac{W(a) - W(x)}{W(a) - W(z)}$$

$$= \sum_{x \sim a} \frac{I(a \vec{x})}{c(a)(W(a) - W(z))}$$

$$P_a(\tau_z < \tau_a^+)$$

$$= \sum_{x \sim a} \frac{I(a \vec{x})}{c(a)(W(a) - W(z))}$$

$$= \frac{\|I\|}{c(a)(W(a) - W(z))}.$$

$$= \frac{1}{c(a)R(a \leftarrow z)}$$

Green's Function

τ is a stopping time.

$$G_\tau(a, x) = E_a(\# \text{ visits to } x \text{ before } \tau).$$

L9.6

$$G_{\tau_z}(a, a) = c(a) R(a \leftrightarrow z)$$


$E(\# \text{ returns to } a \text{ before visiting } z)$

Proof

visits to a is a geometric random variable with parameter $P_a(\tau_z < \tau_a^+)$. $\frac{1}{c(a) R(a \leftrightarrow z)}$

Network Simplification

Parallel Law

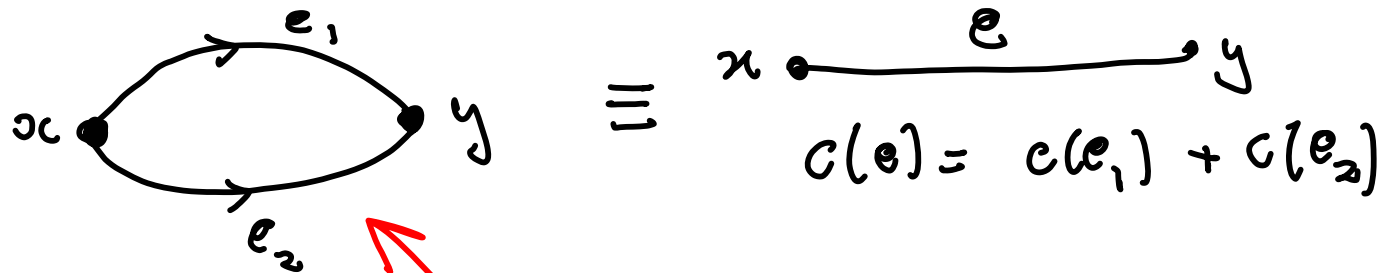


Check:

Ohm's Law: $I(e_i) = [W(y) - W(x)] c(e_i)$

$$I(e) = [W(y) - W(x)] (c(e_1) + c(e_2))$$

Kirchoff law satisfied.

Series Law

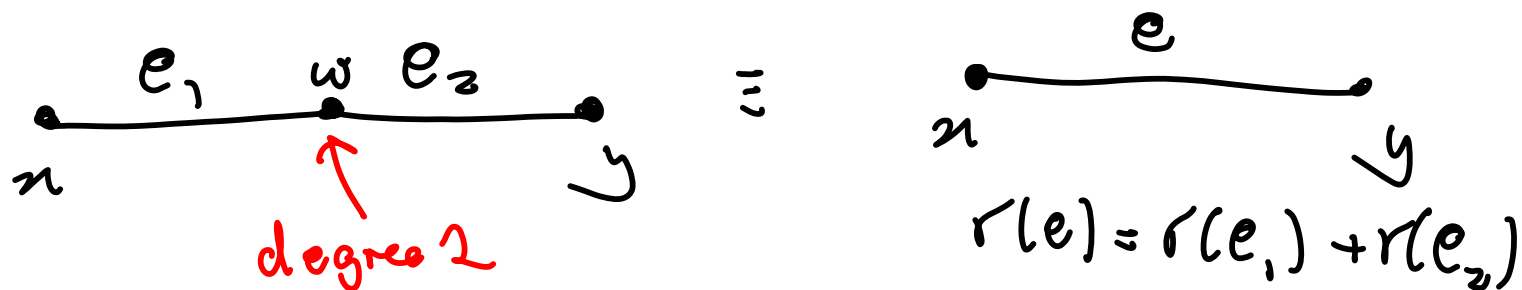

Check: $\frac{W(x) - W(w)}{r(e_1)} = I(e_1)$

||

$= \frac{W(w) - W(y)}{r(e_2)} = I(e_2)$

$\frac{W(x) - W(y)}{r(e)} = I(e)$

$$r(e) = \frac{W(x) - W(y)}{I(e)} = \underbrace{\frac{W(x) - W(w)}{I(e_1)}}_{=} + \underbrace{\frac{W(w) - W(y)}{I(e_2)}}_{=}$$

Gluing


x y



Same voltage
 $W(x) = W(y)$

x, y

Identify vertices
and keep edge.

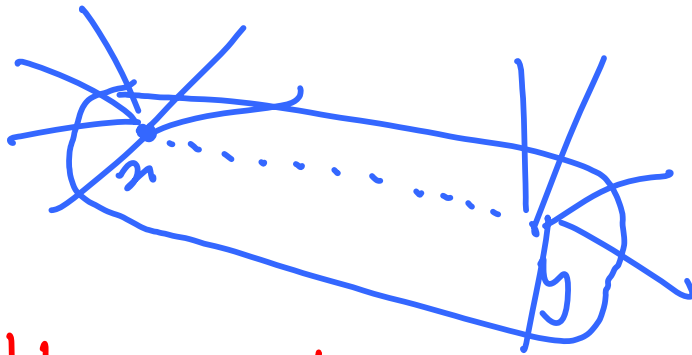


Voltages unchanged
 $\Rightarrow$ Current unchanged.

Ex 9.7

Path a to $z = a_0, a_1, \dots, a_k$

$$W(a_i) = 1 - \frac{i}{k}$$

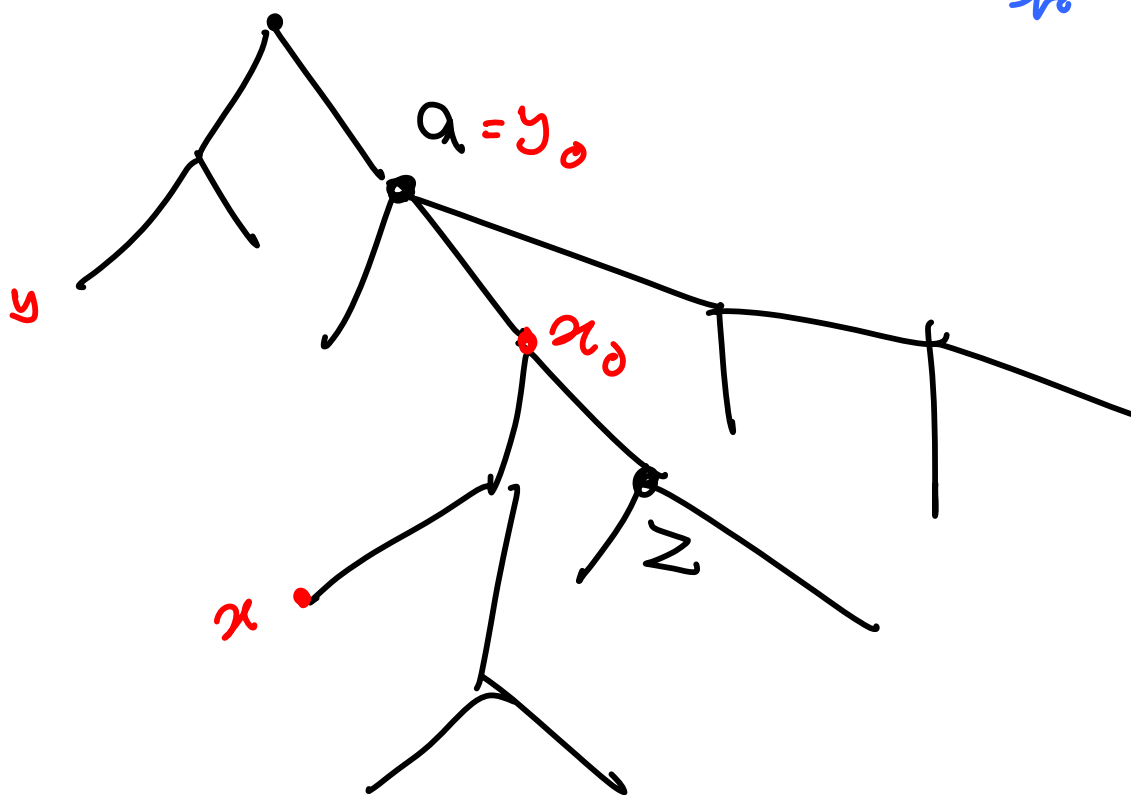

$$(i) R(a \leftrightarrow z) = d(a, z)$$

$$(ii) W(x) = W(x_0)$$